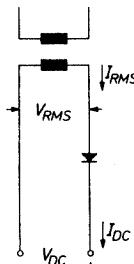


Technical Information


Design Information for Single-Phase Circuits

Circuit Diagrams


Half-wave



Full-wave

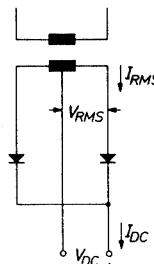

Bridge

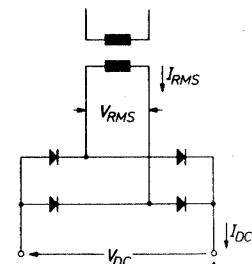

Resistive load

Characteristics (each diode):

$$\begin{aligned} V_{RRM} &> 3.45 \cdot V_{DC} \\ V_{RRM} &> 1.56 \cdot V_{RMS} \\ I_{FAV} &> 1.0 \cdot I_{DC} \end{aligned}$$

$$\begin{aligned} 3.45 \cdot V_{DC} \\ 3.12 \cdot V_{RMS} \\ 0.5 \cdot I_{DC} \end{aligned}$$

$$\begin{aligned} 1.73 \cdot V_{DC} \\ 1.56 \cdot V_{RMS} \\ 0.5 \cdot I_{DC} \end{aligned}$$

Circuit parameters:

$$\begin{aligned} V_{RMS} & 2.22 \cdot V_{DC} \\ I_{RMS} & 1.57 \cdot I_{DC} \\ P_t & 3.1 \cdot P_{DC} \\ V_{BR} & 1.21 \cdot V_{DC} \\ f_{BR} & 1 \cdot f_{in} \end{aligned}$$

$$\begin{aligned} 1.11 \cdot V_{DC} \\ 0.78 (0.71) \cdot I_{DC} \\ 1.48 (1.34) \cdot P_{DC} \\ 0.48 \cdot V_{DC} \\ 2 \cdot f_{in} \end{aligned}$$

$$\begin{aligned} 1.11 \cdot V_{DC} \\ 1.11 (1.0) \cdot I_{DC} \\ 1.24 (1.11) \cdot P_{DC} \\ 0.48 \cdot V_{DC} \\ 2 \cdot f_{in} \end{aligned}$$

Load with back EMF

Characteristics (each diode):

$$\begin{aligned} V_{RRM} &> 2.65 \cdot V_{DC} \\ V_{RRM} &> 3.12 \cdot V_{RMS} \end{aligned}$$

$$\begin{aligned} 2.5 \cdot V_{DC} \\ 3.12 \cdot V_{RMS} \end{aligned}$$

$$\begin{aligned} 1.25 \cdot V_{DC} \\ 1.56 \cdot V_{RMS} \end{aligned}$$

Circuit parameters:

$$\begin{aligned} V_{RMS} & 0.85 \cdot V_{DC} \\ I_{RMS} & 2.1 \cdot I_{DC} \\ P_t & 1.73 \cdot P_{DC} \\ V_{BR} & \text{to } 0.05 \cdot V_{DC} \\ f_{BR} & 1 \cdot f_{in} \end{aligned}$$

$$\begin{aligned} 0.8 \cdot V_{DC} \\ 1.1 \cdot I_{DC} \\ 1.48 \cdot P_{DC} \\ \text{to } 0.05 \cdot V_{DC} \\ 2 \cdot f_{in} \end{aligned}$$

$$\begin{aligned} 0.8 \cdot V_{DC} \\ 1.57 \cdot I_{DC} \\ 1.24 \cdot P_{DC} \\ \text{to } 0.05 \cdot V_{DC} \\ 2 \cdot f_{in} \end{aligned}$$

Values in brackets apply to circuits with resistive loads and incorporating a high inductance choke.